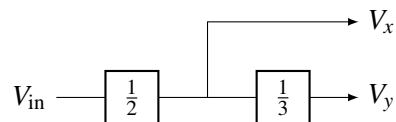


# EECS 16A    Designing Information Devices and Systems I

## Discussion 12A

### 1. Modular Circuit Buffer


Let's try designing circuits that perform a set of mathematical operations using op-amps. While voltage dividers on their own cannot be combined without altering their behavior, op-amps can preserve their behavior when combined and thus are a perfect tool for modular circuit design. We would like to implement the block diagram shown below:



In other words, create a circuit with two outputs  $V_x$  and  $V_y$ , where  $V_x = \frac{1}{2}V_{in}$  and  $V_y = \frac{1}{3}V_x = \frac{1}{6}V_{in}$ .

- (a) Draw two voltage dividers, one for each operation (the  $1/2$  and  $1/3$  scalings). What relationships hold for the resistor values for the  $1/2$  divider, and for the resistor values for the  $1/3$  divider?

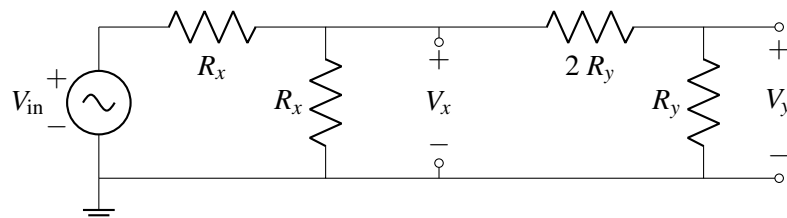- (b) If you combine the voltage dividers, made in part (a), as shown by the block diagram (output of the  $1/2$  voltage divider becomes the source for the  $1/3$  voltage divider circuit), do they behave as we hope (meaning  $V_{in} = 2V_x = 6V_y$ )?




(c) Perhaps we could use an op-amp (in negative-feedback) to achieve our desired behavior.

Modify the implementation you tried in part (b) using a negative feedback op-amp in order to achieve the desired  $V_x, V_y$  relations  $V_x = \frac{V_{in}}{2}$  and  $V_y = \frac{V_x}{3} = \frac{V_{in}}{6}$ .


HINT: Place the op-amp in between the dividers such that the  $V_x$  node is an input into the op-amp, while the source of the 2nd divider is the output of the op-amp!
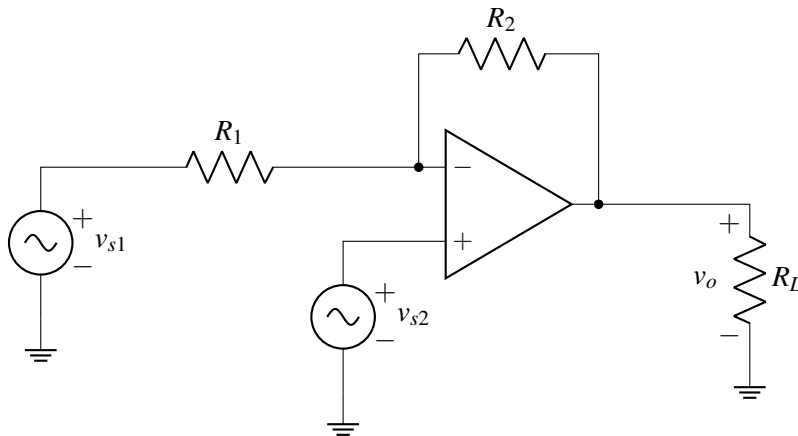
## 2. Amplifier with Multiple Inputs


In this problem we will use superposition and the Golden Rules to find the output of the following op amp circuit with multiple inputs:



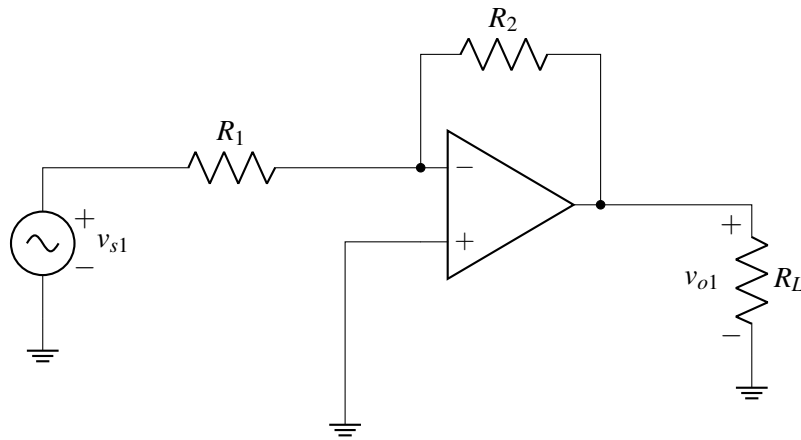
(a) First, let's turn off  $v_{s2}$ . Use the **Golden Rules** to find  $v_{o1}$  for the circuit below.



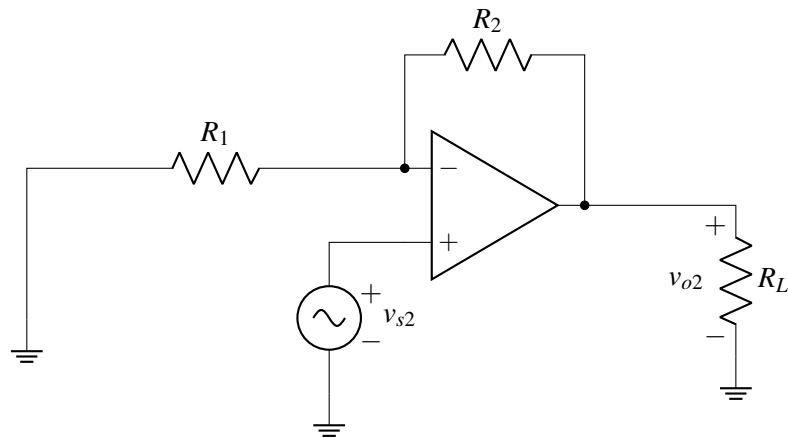(b) Now let's turn off  $v_{s1}$ . Use the **Golden Rules** to find  $v_{o2}$  for the circuit below.



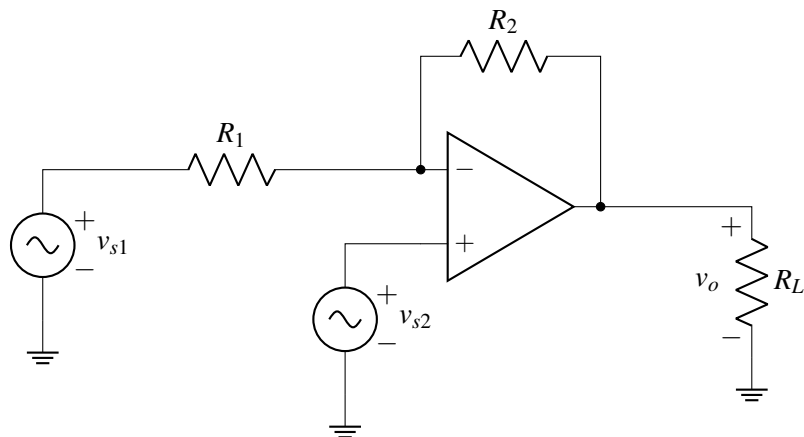(c) Use **superposition** to find the output voltage  $v_o$  for the circuit shown below.



### 3. Modular Op-Amp Circuits

Let's design blocks that implement the following operations:

- (a) Scale the input voltage so that:  $V_{\text{out}} = +5 V_{\text{in}}$ .
- (b) Scale and invert the input voltage so that:  $V_{\text{out}} = -2 V_{\text{in}}$ .