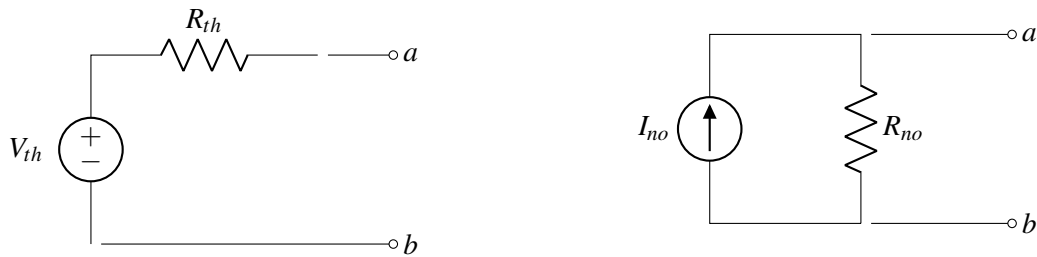

EECS 16A Designing Information Devices and Systems I

Discussion 9A


1. Thevenin and Norton Equivalence

The general Thévenin and Norton equivalents are shown below:




Find the Thévenin and Norton equivalents across terminals a and b for the circuits given below.


(a)

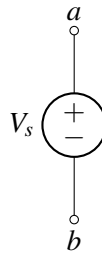


(b)

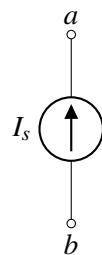


(c)

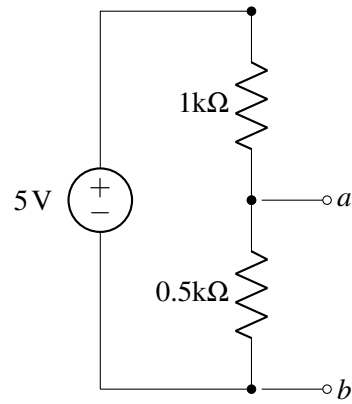


(d)

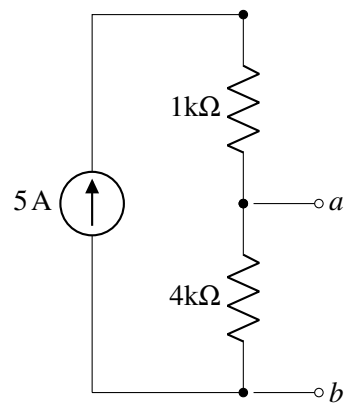


(e)

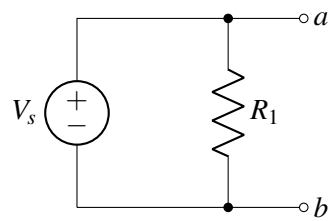

(f)

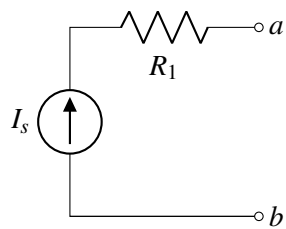

(g)

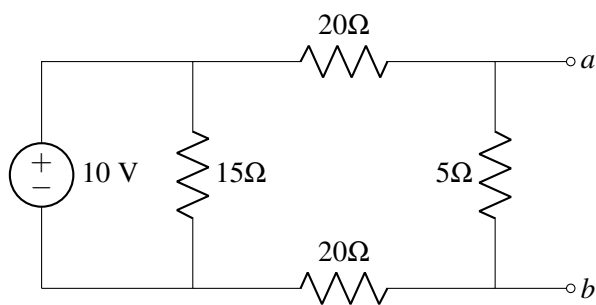

2. Series and Parallel Combinations

For the resistor network shown below, find an equivalent resistance between the terminals A and B using the resistor combination rules for series and parallel resistors.

